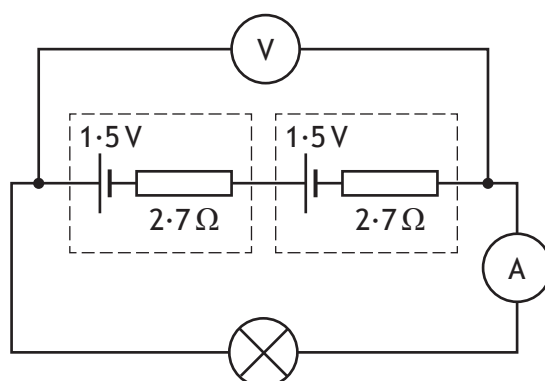


12. A lamp is connected to a battery containing two cells as shown.




The e.m.f. of each cell is 1.5 V and the internal resistance of each cell is $2.7\ \Omega$.
The reading on the ammeter is 64 mA .

- (a) State what is meant by an e.m.f. of 1.5 V . 1
- (b) (i) Show that the lost volts in the battery is 0.35 V . 2
Space for working and answer
- (ii) Determine the reading on the voltmeter. 1
Space for working and answer
- (iii) Calculate the power dissipated by the lamp. 3
Space for working and answer

12. (continued)

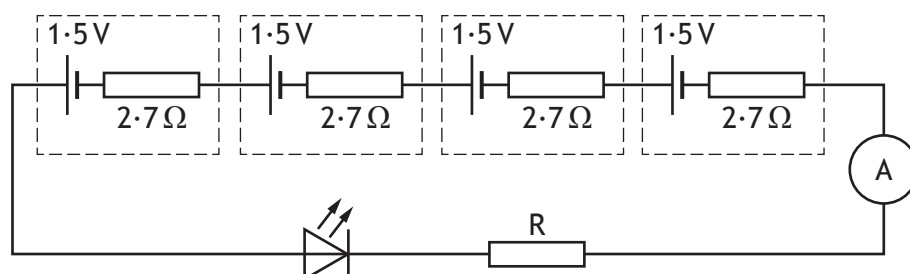- (c) In a different circuit, an LED is connected to a battery containing four cells.



The potential difference across the LED is 3.6 V when the current is 26 mA.
Determine the resistance of resistor R.

4

Space for working and answer

