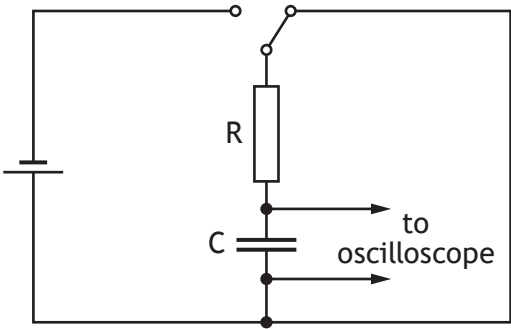


19. The circuit shown is used to charge and then discharge a capacitor C.



Which pair of graphs shows how the potential difference V across the capacitor varies with time t during charging and discharging?

