
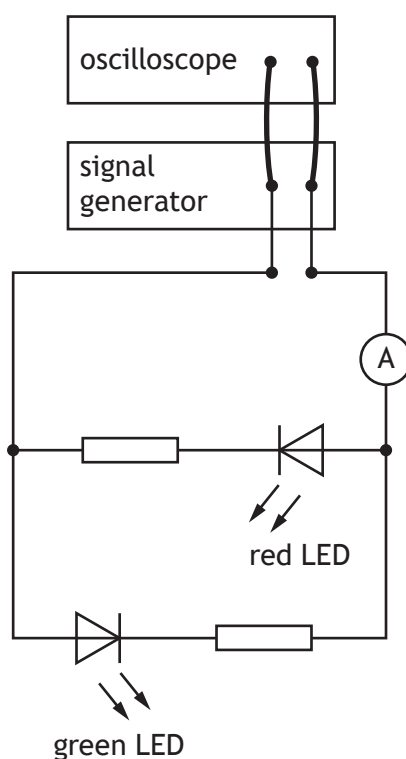


12. A student carries out a series of experiments to investigate alternating current.

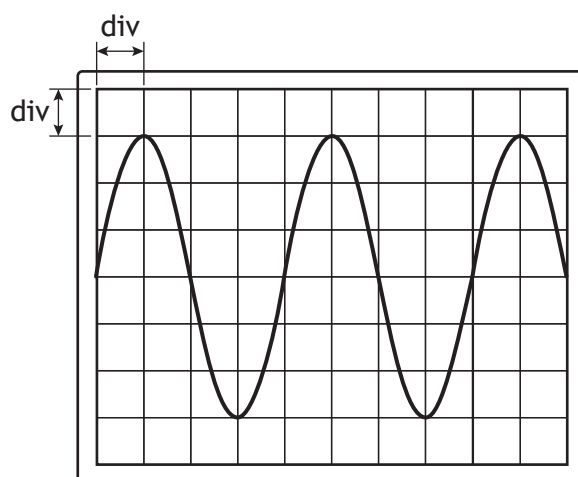(a) A signal generator is connected to an oscilloscope and a circuit as shown.



The output of the signal generator is displayed on the oscilloscope.



The Y-gain setting on the oscilloscope is 1.0 V/div .

The timebase setting on the oscilloscope is 0.5 s/div .

12. (a) (continued)

- (i) Determine the peak voltage of the output of the signal generator.

1

Space for working and answer

- (ii) Determine the frequency of the output of the signal generator.

3

Space for working and answer

- (iii) The student observes that the red LED is only lit when the ammeter gives a positive reading and the green LED is only lit when the ammeter gives a negative reading.

Explain these observations.


2



* X 7 5 7 7 6 0 1 3 9 *

12. (continued)

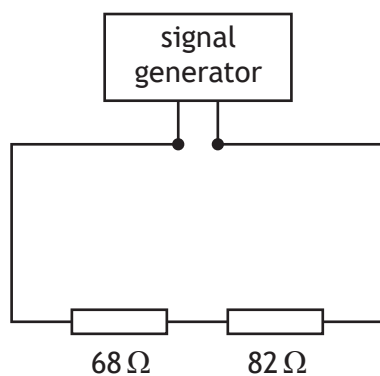- (b) The signal generator is now connected in a circuit as shown.
The settings on the signal generator are unchanged.
The signal generator has negligible internal resistance.



Determine the r.m.s. voltage across the 82 Ω resistor.
Space for working and answer

5

