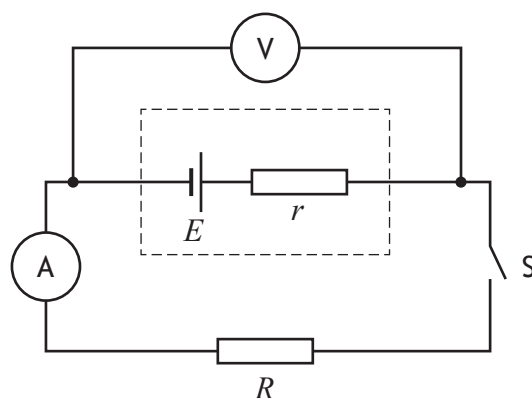


12. (a) A student sets up the circuit shown.



When switch S is open the reading on the voltmeter is 1.5 V .

Switch S is now closed.

The reading on the voltmeter is now 1.3 V and the reading on the ammeter is 0.88 A .

- (i) State the EMF E of the cell.

1

- (ii) Calculate the internal resistance r of the cell.

3

Space for working and answer

- (iii) Explain why the reading on the voltmeter decreases when the switch is closed.


2



* X 8 5 7 7 6 0 1 3 0 *

12. (continued)

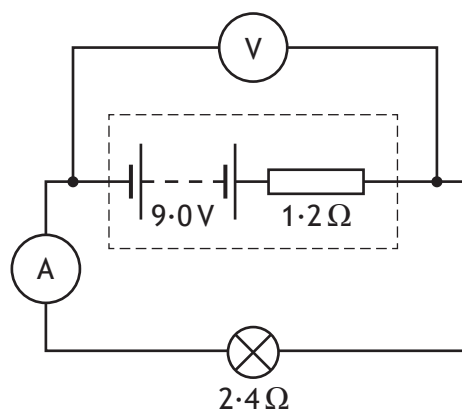- (b) A battery of EMF 9.0 V and internal resistance $1.2\ \Omega$ is connected in series with a lamp. The lamp has a resistance of $2.4\ \Omega$.



- (i) Determine the current in the lamp.

3

Space for working and answer

- (ii) Calculate the power dissipated in the lamp.

3

Space for working and answer



* X 8 5 7 7 6 0 1 3 1 *