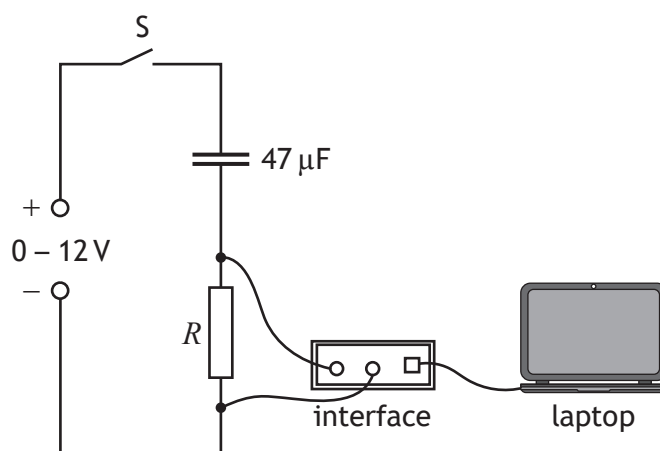


13. A student investigates the charging of a capacitor.  
The student sets up the circuit as shown using a  $47\ \mu\text{F}$  capacitor.




The capacitor is initially uncharged. The switch  $S$  is now closed. A laptop connected to an interface displays a graph of current against time as the capacitor charges.

- (a) The variable voltage supply is set at  $6.0\text{V}$ .  
Calculate the maximum charge stored by the capacitor.  
*Space for working and answer*

3

13. (continued)

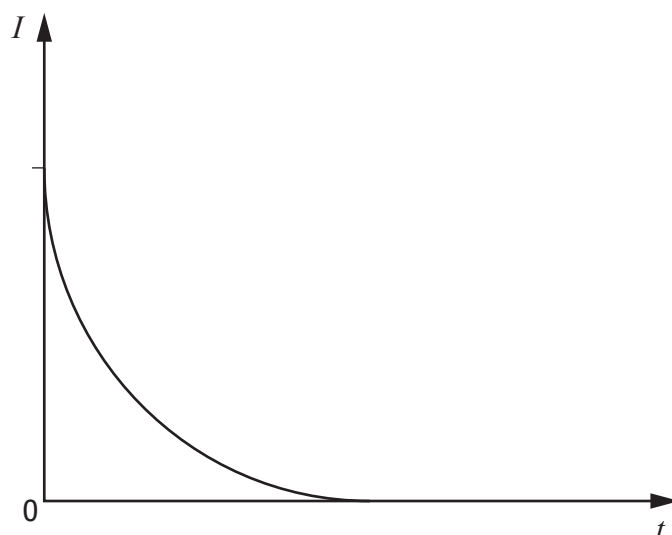- (b) The graph shows how the current  $I$  varies with time  $t$  as the capacitor charges.



Switch S is opened, and the capacitor is discharged.

The resistor is now replaced with one that has a greater resistance.

Switch S is again closed and the capacitor charges.

Add a line to the graph above to show how the current now varies with time as the capacitor charges.

2

(An additional graph, if required, can be found on *page 45*.)

- (c) Suggest an alteration the student could make to this circuit to increase the maximum energy stored by the  $47\ \mu\text{F}$  capacitor.

1

[Turn over




\* X 8 5 7 7 6 0 1 3 3 \*

13. (continued)

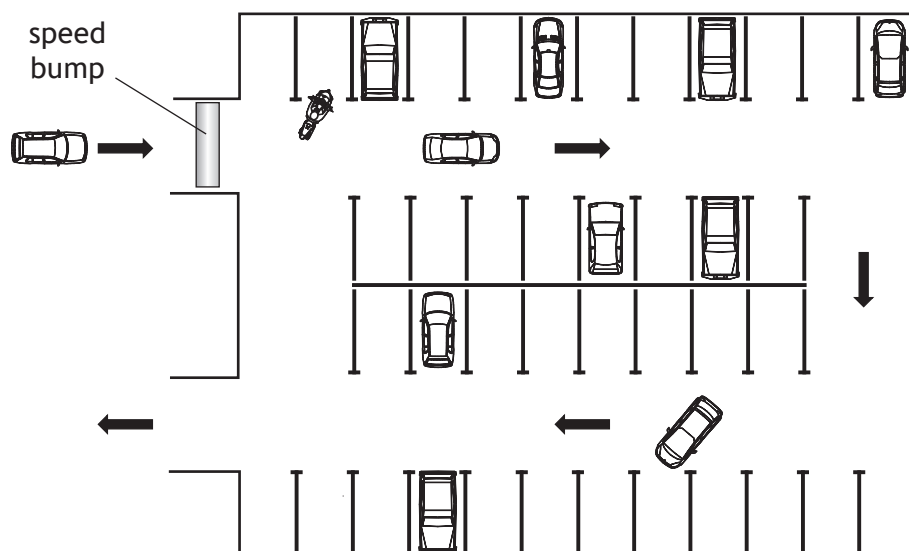- (d) The use of analogies from everyday life can help improve the understanding of physics concepts.

Vehicles using a car park may be taken as an analogy for the charging of a capacitor.



Use your knowledge of physics to comment on this analogy.

3