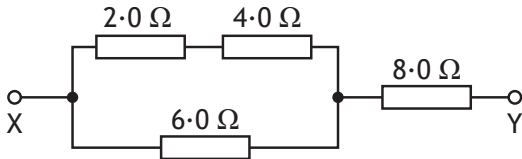


21. Four resistors are connected as shown.



The total resistance between X and Y is

- A  $1.0\ \Omega$
- B  $8.9\ \Omega$
- C  $9.1\ \Omega$
- D  $11\ \Omega$
- E  $20\ \Omega$ .