

22. A resistor of resistance $100\ \Omega$ is rated at 4 W.

The maximum voltage which can be applied across the resistor without exceeding its power rating is

A 0.04 V

B 5 V

C 20 V

D 25 V

E 400 V.