


13. A student connects a signal generator, which provides an alternating current, to an oscilloscope.



- (a) State what is meant by an *alternating current*.

1

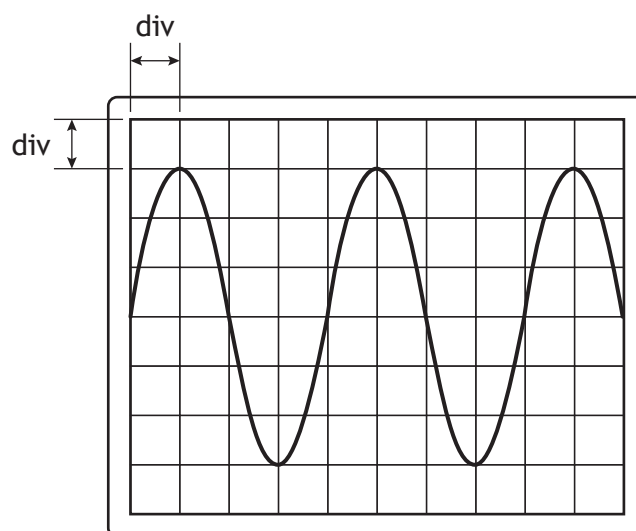- (b) The oscilloscope screen shows the output of the signal generator.



The Y-gain setting on the oscilloscope is 5.0 V/div.

The timebase setting on the oscilloscope is 1.0 ms/div.

- (i) Determine the peak voltage of the output of the signal generator.

1

Space for working and answer



* X 8 5 7 7 6 0 1 3 4 *


13. (b) (continued)

- (ii) Determine the frequency of the output of the signal generator.

3

Space for working and answer

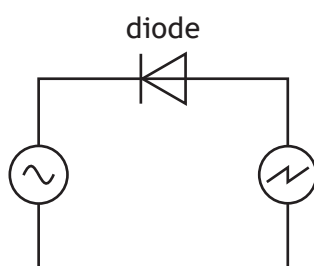- (c) The student connects a diode to the circuit as shown. The settings on the signal generator and the oscilloscope are unchanged.




Current can only flow in one direction through a diode.

This changes the trace on the oscilloscope screen.

On the diagram below, draw the new trace seen on the oscilloscope screen.

2

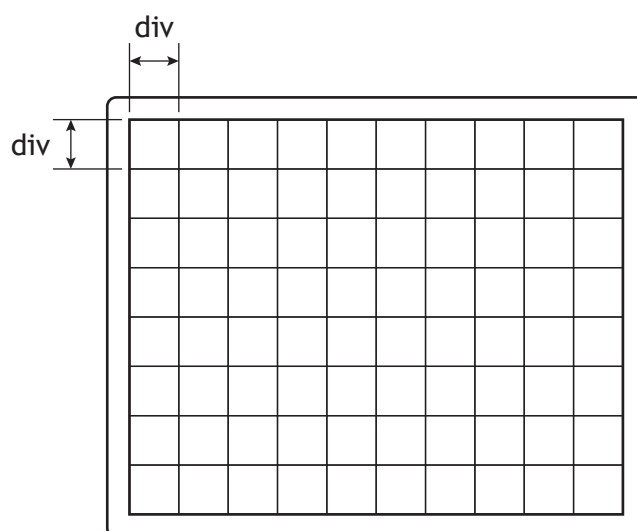

(An additional diagram, if required can be found on page 45.)

