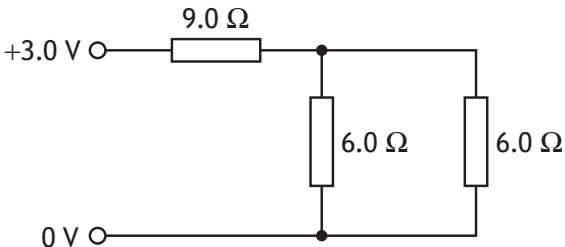


19. Three resistors are connected to a 3.0 V power supply as shown.



The power supply has negligible internal resistance.

The power dissipated in the circuit is:

- A 0.25 W
- B 0.43 W
- C 0.75 W
- D 2.1 W
- E 4.0 W.