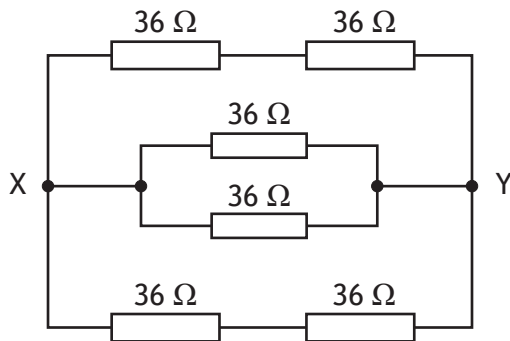


20. Six $36\ \Omega$ resistors are connected as shown.



The total resistance between points X and Y is

- A $6.0\ \Omega$
- B $8.0\ \Omega$
- C $12\ \Omega$
- D $18\ \Omega$
- E $24\ \Omega$.