

## 2017 H2 Q12

Section: Electricity

Topic: e.m.f., internal resistance, terminal p.d., power

Two identical cells in the battery: e.m.f. 1.5 V each, internal resistance  $2.7\ \Omega$  each. Circuit current (ammeter) is 64 mA. Voltmeter is across the lamp.

### **(a) Meaning of an e.m.f. of 1.5 V**

The e.m.f. is the energy supplied per coulomb of charge by the cell. An e.m.f. of 1.5 V means the cell provides 1.5 J of energy to each coulomb of charge passing through it.

### **(b)(i) Lost volts in the battery**

Lost volts = current  $\times$  total internal resistance.

$$\text{Total internal resistance} = r_{\text{total}} = r_1 + r_2 = 2.7 + 2.7 = 5.4\ \Omega.$$

$$\text{Lost volts} = I r_{\text{total}} = 0.064 \times 5.4 = 0.3456\ \text{V} \approx 0.35\ \text{V}.$$

**Answer: 0.35 V**

### **(b)(ii) Voltmeter reading (terminal p.d. across lamp)**

$$\text{Total e.m.f. of the battery} = 1.5 + 1.5 = 3.0\ \text{V}.$$

Terminal p.d. =  $E_{\text{total}} - \text{lost volts} = 3.0 - 0.3456 = 2.6544 \text{ V}$ .

**Answer:  $\approx 2.65 \text{ V}$**

**(b)(iii) Power dissipated by the lamp**

$P = VI$  across the lamp.

$$P = 2.6544 \times 0.064 = 0.1699 \text{ W}.$$

**Answer:  $\approx 0.17 \text{ W}$**

### **Revision tips**

- Lost volts =  $I r_{\text{internal}}$ ; terminal p.d. =  $E - Ir$ .
- In series: e.m.f.s add; internal resistances add.
- Power in a component:  $P = VI = I^2R = V^2/R$  (use whichever data are given).