

2017 H2 Q13

Section: Electricity

Topic: Capacitors — time constant, initial current, effect of circuit on τ

An uncharged $220\ \mu\text{F}$ capacitor is connected with resistors (two $6800\ \Omega$) and switches $S1$ and $S2$ to a $12\ \text{V}$ supply (negligible internal resistance).

(a) Initial charging current when $S1$ is closed (charging time $\approx 7.5\ \text{s}$)

For RC charging, a capacitor is effectively 'fully charged' after about 5 time constants ($\approx 5\tau$). Given charging time $7.5\ \text{s}$, take $\tau \approx 7.5/5 = 1.5\ \text{s}$.

$$\tau = RC \Rightarrow R = \tau/C = 1.5 / (220 \times 10^{-6}) \approx 6.8 \times 10^3\ \Omega.$$

$$\text{Initial charging current } I_0 = V/R = 12 / 6.8 \times 10^3 \approx 1.8 \times 10^{-3}\ \text{A}.$$

Answer: $I_0 \approx 1.8\ \text{mA}$

(b) Why charging time is less when $S2$ is closed before $S1$

Closing $S2$ alters the charging path resistance (e.g. bypasses one resistor or adds a parallel path). This reduces the effective resistance in series with the capacitor, so the time constant $\tau = RC$ is smaller. Therefore the capacitor reaches full charge in less time than in part (a).

Revision tips

- Rule of thumb: 'fully charged' ≈ 5 time constants (5τ).
- Initial current in RC charging: $I_0 = V/R$ (at $t = 0$).
- Reducing the series resistance reduces the time constant and speeds up charging/discharging.