2018 Ph H2 Q12

Section: Electricity

Topic: Alternating current, oscilloscopes, RMS

voltage

- (a)(i) From oscilloscope trace with Y-gain 1 V/div, determine peak voltage.
- (ii) From timebase 0.5 s/div and waveform, determine frequency.
- (iii) Explain why red LED lights for positive current, green LED for negative.
- (b) Signal generator connected to series resistors 68 Ω and 82 Ω . Determine the r.m.s. voltage across the 82 Ω resistor.

Worked solution

(a)(i)

Peak = number of vertical divisions \times Y-gain.

 $= 3.0 \times 1.0 V = 3.0 V.$

Answer: 3.0 V

(a)(ii)

Period $T = number of horizontal divisions \times timebase.$

 $= 4.0 \times 0.5 \text{ s} = 2.0 \text{ s}.$

Frequency f = 1/T = 0.50 Hz.

Answer: 0.50 Hz

(a)(iii)

LEDs conduct only in one direction (they are diodes). During the positive half-cycle, current flows forward through the red LED, so it lights. During the negative half-cycle, current direction reverses, forward biasing the green LED instead. Thus they light alternately depending on current direction.

Answer: Red LED lit in positive half-cycle, green in negative

(b)

Peak voltage across whole circuit = 3.0 V.

RMS voltage across whole circuit = $Vp/\sqrt{2} = 3.0/\sqrt{2} = 2.12 \text{ V}$.

Voltage divides in proportion to resistance: $V_{82} = V_{total} \times (82/(68+82))$.

 $= 2.12 \times 82/150 = 1.16 \text{ V}.$

Answer: 1.16 V

Final answers

$$(a)(i) Vp = 3.0 V$$

$$(a)(ii) f = 0.50 Hz$$

(a)(iii) Red LED lit in positive cycle, green in negative cycle

(b)
$$V_rms$$
 across 82 $\Omega = 1.16 V$

Revision tips

- Oscilloscope: peak voltage = vertical divisions × Y-gain.
- Frequency = 1/period; period from horizontal divisions × timebase.
- LEDs conduct only in forward bias, so each lights in alternate half-cycles.
- RMS voltage = $Vp/\sqrt{2}$ for sine wave.
- Series resistors divide voltage in proportion to resistance.