

## 2019 Ph H1 Q23

Section: Electricity

Topic: Current, PD, Power, Resistance

Question Summary

A 6.0 V battery is connected across two resistors in parallel: 3.0  $\Omega$  and 6.0  $\Omega$ . What power is dissipated in the 3.0  $\Omega$  resistor?

Worked Solution

In parallel, each branch has the full 6.0 V.

$$P = V^2/R = (6.0)^2/3.0 = 12 \text{ W.}$$

Cross-check:  $I = V/R = 2 \text{ A}$ ,  $P = VI = 6 \times 2 = 12 \text{ W}$ .

Final Answer: D

Revision Tips

- Parallel: same voltage across each branch.
- Use  $P = V^2/R$  for a quick calculation.
- Cross-check with  $P = VI$  or  $P = I^2R$ .