

2021 Ph H1 Q21

Section: Electricity

Topic: Current, PD, Power, Resistance

Question Summary

Between X and Y: an $8\ \Omega$ resistor in series with a parallel network. Upper branch: $2\ \Omega + 4\ \Omega$ (series = $6\ \Omega$). Lower branch: $6\ \Omega$. Find total resistance.

Worked Solution

Upper branch: $2 + 4 = 6\ \Omega$.

Parallel: $1/R_p = 1/6 + 1/6 = 1/3 \Rightarrow R_p = 3\ \Omega$.

Add series $8\ \Omega$: $R_{\text{total}} = 3 + 8 = 11\ \Omega$.

Final Answer: D

Revision Tips

- Series: add resistances.
- Parallel: reciprocals.
- Equal resistors in parallel halve the resistance.