

2022 Ph H1 Q19

Section: Electricity

Topic: Current, PD, Power, Resistance

Question Summary

Three resistors are connected to a 3.0 V supply: a 9.0 Ω in series with a parallel combination of two 6.0 Ω resistors. Find the total power dissipated in the circuit.

Worked Solution

Parallel pair: $R_p = (6 \times 6)/(6 + 6) = 36/12 = 3.0 \Omega$.

Series total: $R_{\text{total}} = 9.0 + 3.0 = 12.0 \Omega$.

Circuit current: $I = V/R = 3.0 / 12.0 = 0.25 \text{ A}$.

Power: $P = VI = 3.0 \times 0.25 = 0.75 \text{ W}$.

Final Answer: C

Revision Tips

- Combine parallel first (use product over sum for two resistors).
- Total power for whole circuit can be found by $P = VI$ using supply V and total I.
- Cross-check: $P = V^2/R_{\text{total}} = 9 / 12 = 0.75 \text{ W}$ (same result).