

2022 Ph H1 Q20

Section: Electricity

Topic: Current, PD, Power, Resistance

Question Summary

Six resistors, each $5\ \Omega$, are connected to a $12\ \text{V}$ supply as shown in the paper. Points X and Y lie across part of the network. Which row gives the total circuit resistance and the p.d. across X-Y?

Worked Solution

By simplifying the network, the circuit reduces to three equal $5\ \Omega$ sections in series, giving a total resistance of $15\ \Omega$. With a $12\ \text{V}$ supply:

Total current, $I = V/R = 12 / 15 = 0.80\ \text{A}$.

Each $5\ \Omega$ section in series therefore drops $V = IR = 0.80 \times 5 = 4.0\ \text{V}$.

Section X-Y spans one of these $5\ \Omega$ sections, so the potential difference across X-Y is $4.0\ \text{V}$.

Final Answer: B

Revision Tips

- Look for symmetry to regroup resistors into simple series sections.
- Once in series, the same current flows and voltages divide proportionally to resistance.
- Use $I = V/R_{\text{total}}$ and $V_{\text{section}} = I \times R_{\text{section}}$ to get section voltages.