

2022 Ph H1 Q22

Section: Electricity

Topic: Capacitors

Question Summary

A $220\ \mu\text{F}$ capacitor is connected in a circuit with a $12\ \text{V}$ battery (negligible internal resistance) and a switch, as shown on the paper. The capacitor is initially uncharged. When the reading on the voltmeter is $7.0\ \text{V}$, what is the charge stored on the capacitor?

Worked Solution

Interpret the diagram: the voltmeter is across the resistor, not the capacitor. So the capacitor voltage is $V_C = 12 - 7 = 5.0\ \text{V}$.

Use $Q = C V$.

$$C = 220\ \mu\text{F} = 220 \times 10^{-6}\ \text{F}.$$

$$Q = 220 \times 10^{-6} \times 5.0 = 1.10 \times 10^{-3}\ \text{C}.$$

Final Answer: C

Revision Tips

- Read circuit symbols carefully — where is the voltmeter connected?
- $Q = C V$ gives instantaneous charge for a given capacitor voltage.
- Convert $\mu\text{F} \rightarrow \text{F}$ before substituting.