

## 2022 Ph H1 Q23

Section: Electricity

Topic: Capacitors (RC charging)

Question Summary

A series RC circuit is connected to a d.c. supply at  $t = 0$ . Which set of graphs correctly shows how the resistor voltage  $V_R$ , the capacitor voltage  $V_C$ , and the current  $I$  vary with time as the capacitor charges?

Worked Solution

Charging behaviour for RC circuits:

- $I$  starts maximum and decays exponentially to 0.
- $V_R = I R$ , so it also decays exponentially from its initial maximum to 0.
- $V_C$  rises exponentially from 0 to the supply voltage.

Select the option whose three graphs match these shapes ( $I \downarrow \exp$  to 0,  $V_R \downarrow \exp$  to 0,  $V_C \uparrow \exp$  to  $V$ ).

Final Answer: E

Revision Tips

- At  $t = 0^+$ , the uncharged capacitor behaves like a short:  $I$  is largest,  $V_R \approx \text{supply}$ ,  $V_C \approx 0$ .
- As  $t \rightarrow \infty$ , the capacitor is open-circuit:  $I \rightarrow 0$ ,  $V_R \rightarrow 0$ ,  $V_C \rightarrow \text{supply}$ .
- Link  $V_R(t)$  to  $I(t)$  via Ohm's law:  $V_R = I R$ .