

2022 Ph H2 Q12

Section: Electricity

Topic: Sources & Internal Resistance

Student investigates EMF and internal resistance from V-I graph. (a) Define EMF. (b) Use graph to find EMF and r . (c) How to measure EMF directly. (d) Explain why terminal PD decreases as R decreases. (e) Sketch line for smaller EMF, same r .

Worked solution

(a) EMF is the energy supplied by a source to each coulomb of charge, when no current is drawn (open circuit).

(b)

(i) From graph, intercept at $I=0$ gives $E \approx 6.0 \text{ V}$.

(ii) Slope = $-r$, using $\Delta V/\Delta I$:
 $(6.0 - 2.0) / (0.0 - 0.40) = -10 \Omega$.

Answer: $E = 6.0 \text{ V}$, $r = 10 \Omega$

(c) To measure EMF directly, open the switch so no current flows. Measure the potential difference across the battery with a voltmeter.

(d) Decreasing R increases current. Voltage lost across internal resistance (Ir) increases, so terminal PD ($V = E - Ir$) decreases.

(e) A smaller EMF but same r gives a straight line with:

- Same gradient ($-r$)
- Lower intercept on V axis.

Graph shifts downward, parallel to original line.

Final answers

(a) EMF = energy per coulomb, no current

(b)(i) $E = 6.0 \text{ V}$

(b)(ii) $r = 10 \text{ } \Omega$

(c) Open circuit voltmeter reading

(d) Increased current \Rightarrow larger $Ir \Rightarrow$ smaller V

(e) Line parallel, lower intercept

Revision tips

- $V-I$ graph: intercept = EMF, slope = $-r$.
- Internal resistance causes lost volts Ir inside battery.
- Open circuit voltmeter reading gives EMF directly.
- Reducing load resistance increases current, increasing lost volts.
- For smaller EMF, line is parallel but lower intercept.