

2022 Ph H2 Q13

Section: Electricity

Topic: Capacitors

Experiment investigating charging of capacitor. (a) Describe how results are obtained and used to show V vs t . (b) Capacitor $47\ \mu\text{F}$ charged to $12\ \text{V}$: (i) calculate maximum energy, (ii) suggest alteration to increase stored energy.

Worked solution

(a) Close switch S , start stopwatch at same time. Take repeated readings of capacitor voltage V using voltmeter at regular time intervals. Plot graph of V vs t to show the exponential charging curve. Alternatively, data logger could be used to record V continuously against t .

(b)(i) Maximum energy

$$\begin{aligned} E &= \frac{1}{2} C V^2 \\ &= 0.5 \times 47 \times 10^{-6} \times (12)^2 \\ &= 3.38 \times 10^{-3} \text{ J} \end{aligned}$$

Answer: $3.4 \times 10^{-3} \text{ J}$

(b)(ii) To increase maximum energy ($E = \frac{1}{2} C V^2$), increase either capacitance C or supply voltage V . For example, raise supply voltage above $12\ \text{V}$ (if within capacitor rating).

Final answers

(a) Record V vs t , plot charging curve

(b)(i) $E = 3.4 \times 10^{-3} \text{ J}$

(b)(ii) Increase capacitance or voltage supply

Revision tips

- Charging follows exponential: $V(t) = V_{\text{max}}(1 - e^{(-t/RC)})$.
- Energy stored in capacitor: $\frac{1}{2} C V^2$.
- Increasing supply voltage or capacitance increases stored energy.
- Use of stopwatch and voltmeter allows manual data collection.
- Capacitor fully charged when current falls to zero and $V = \text{supply voltage}$.