

2023 Ph H2 Q12

Section: Electricity

Topic: Internal Resistance

Summary of Question:

Battery of emf 12 V and internal resistance r is connected to three $16\ \Omega$ resistors in parallel (part a). Ammeter reads 0.38 A. (i) Calculate terminal p.d. of the battery. (ii) Calculate internal resistance r . (iii) Calculate power dissipated in internal resistance. (b) Circuit is rearranged (resistors in series/parallel different). State whether power dissipated in r is greater than, equal to, or less than before, and justify.

(a)(i) Terminal potential difference

t.p.d. = emf – Ir = V . Total current $I = 0.38$ A flows.
Equivalent resistance of external circuit ($3 \times 16\ \Omega$ in parallel) = $16/3 = 5.33\ \Omega$. So terminal p.d. = $I \times R = 0.38 \times 5.33 = 2.03$ V.

(a)(ii) Internal resistance

Using emf = $V + Ir \rightarrow r = (\text{emf} - V)/I = (12.0 - 2.03)/0.38 = 26.2\ \Omega$.

(a)(iii) Power dissipated in r

$P = I^2r = (0.38)^2 \times 26.2 = 3.79$ W.

(b) Rearranged circuit

Now the three $16\ \Omega$ resistors are in series-parallel with higher external resistance than before. This reduces the current drawn from the battery. Since $P = I^2r$, the power dissipated in the internal resistance is less than before.

Final Answers

(a)(i) Terminal p.d. = $2.03\ \text{V}$

(a)(ii) Internal resistance $r = 26.2\ \Omega$

(a)(iii) Power in $r = 3.79\ \text{W}$

(b) Power dissipated in r is less than before (because external resistance increases, reducing current).

Revision Tips

- Terminal p.d. = $\text{emf} - Ir$; also equal to current \times external resistance.
- Equivalent resistance of parallel resistors: $1/R = 1/R_1 + 1/R_2 + 1/R_3$.
- Power dissipated in internal resistance = I^2r ; decreases if total current decreases.