

2024 Ph H1 Q18

Section: Electricity

Topic: Current, PD, Power, Resistance

Question Summary

A 12 V supply of negligible internal resistance is connected across a 60 Ω resistor in series with a parallel combination of 20 Ω and 30 Ω resistors. Find the potential difference across the 60 Ω resistor.

Worked Solution

Parallel: $R_p = (20 \times 30) / (20 + 30) = 600 / 50 = 12 \Omega$.

Total resistance: $R_T = 60 + 12 = 72 \Omega$.

Circuit current: $I = V / R = 12 / 72 = 0.167 \text{ A}$.

Voltage across 60 Ω : $V = IR = 0.167 \times 60 \approx 10 \text{ V}$.

Final Answer: E

Revision Tips

- When solving, always reduce parallel parts before adding series parts.
- Voltage across a resistor in series = $I \times R$, where I is the total current.
- Double-check by using the voltage divider formula.