

## 2024 Ph H1 Q20

### Section: Electricity

#### Topic: Sources, Internal Resistance

##### Question Summary

A battery is tested using a variable resistor. Measurements of terminal voltage  $V$  and current  $I$  are plotted to give a straight-line  $V$ - $I$  graph. A student states: (I) EMF is 12 V, (II) internal resistance is  $10\ \Omega$ , (III) short-circuit current is 1.2 A. Which statements are correct?

##### Worked Solution

For a source with internal resistance:  $V = E - Ir$  (straight line with intercept  $E$  and slope  $-r$ ).

- Internal resistance: Using points ( $I = 0.20\text{ A}$ ,  $V = 2\text{ V}$ ) and ( $I = 1.20\text{ A}$ ,  $V = 12\text{ V}$ ):  
 $\Delta V / \Delta I = (12 - 2) / (1.20 - 0.20) = 10\text{ V A}^{-1} \Rightarrow r = 10\ \Omega$ . ☐ II correct.
- EMF: From the  $V$ -axis intercept ( $I = 0$ ),  $E \approx 14\text{ V}$  (from the graph), not  $12\text{ V} \Rightarrow$  I false. ☐
- Short-circuit current:  $V = 0 \Rightarrow I_{\text{sc}} = E/r \approx 14/10 = 1.4\text{ A}$ , not  $1.2\text{ A} \Rightarrow$  III false. ☐

Final Answer: B

##### Revision Tips

- On  $V$ - $I$  graphs:  $y$ -intercept gives EMF; the magnitude of the slope gives internal resistance.
- $I$ -intercept (where  $V = 0$ ) gives the short-circuit current  $I_{\text{sc}} = E/r$ .
- Use two well-spaced points on the straight line to compute gradient reliably.