

2024 Ph H1 Q22

Section: Electricity

Topic: Capacitors (RC charging)

Question Summary

A 12 V source, resistor and capacitor produce the shown I-t charging curve. The capacitor is replaced with an uncharged capacitor of greater capacitance and recharged under the same conditions. Which graph shows the new current-time behaviour?

Worked Solution

Charging current in an RC circuit: $I(t) = (V/R) e^{-t/RC}$.

Increasing C increases the time constant $\tau = RC$. The initial current $I(0) = V/R$ is unchanged (same supply and series resistor), but the decay is slower (curve stretches horizontally).

Final Answer: C

Revision Tips

- For larger C , $\tau = RC$ increases \Rightarrow slower decay of current/voltage changes.
- $I(0)$ depends only on V and R , not on C (capacitor initially behaves like a short).
- New I-t curve starts at the same value and falls more slowly.